

Name: Sriram R	SRN: PES1UG20CS435	Section: H
	Date: 08-09-2021	Week Number: 1

1	Implement a 4 bit ripple carry adder using full adder modules.
	<p><b>Program:</b></p> <p><b>d.v :</b></p> <pre>// Module 4-bit ripple carry adder.  module invert(input wire i, output wire o1);     assign o1 = !i; endmodule  module and2(input wire i0, i1, output wire o2);     assign o2 = i0 &amp; i1; endmodule  module or2(input wire i0, i1, output wire o3);     assign o3 = i0   i1; endmodule  module xor2(input wire i0, i1, output wire o4);     assign o4 = i0 ^ i1; endmodule  module nand2(input wire i0, i1, output wire o5);     wire t;     and2 and2_0 (i0, i1, t);     invert invert_0 (t, o5); endmodule  //Module full adder. module fulladd(input wire a, b, cin, output wire sum, cout);     wire [4:0] t;     xor2 x0(a, b, t[0]);     xor2 x1(t[0], cin, sum);      and2 a0(a, b, t[1]);     and2 a1(a, cin, t[2]);</pre>

```

and2 a2(b, cin, t[3]);

or2 o0(t[1], t[2], t[4]);
or2 o1(t[3], t[4], cout);
endmodule

module fulladdR(input wire [3:0] a, b, input wire cin, output wire [3:0] sum, output
wire cout);

    // Instantiate full adder modules here.
    wire [2:0] c;

    fulladd f1(a[0], b[0], cin, sum[0], c[0]);
    fulladd f2(a[1], b[1], c[0], sum[1], c[1]);
    fulladd f3(a[2], b[2], c[1], sum[2], c[2]);
    fulladd f4(a[3], b[3], c[2], sum[3], cout);

endmodule

dtestBench.v :

`timescale 1 ns / 100 ps
`define TESTVECS 8

module tb;
    reg clk, reset;
    reg [3:0] i0, i1; reg cin;
    wire [3:0] o; wire cout;
    reg [8:0] test_vecs [0:(`TESTVECS-1)];
    integer i;
    initial begin $dumpfile("dump1.vcd");
    $dumpvars(0,tb);
    end
    initial begin reset = 1'b1; #12.5 reset = 1'b0; end
    initial clk = 1'b0; always #5 clk =~ clk;
    initial begin
        test_vecs[0] = 9'b000000010;
        test_vecs[1] = 9'b000100010;
        test_vecs[2] = 9'b011100010;
        test_vecs[3] = 9'b000001110;
        test_vecs[4] = 9'b011001111;
    
```

## Week 1: Basic gates

```
test_vecs[5] = 9'b001110011;
test_vecs[6] = 9'b111100011;
test_vecs[7] = 9'b011101110;
end
initial {i0, i1, cin, i} = 0;
fulladdR u0 (i0, i1, cin, o, cout);
initial begin
    #6 for(i=0;i<`TESTVECS;i=i+1)
        begin #10 {i0, i1, cin}=test_vecs[i]; end
    #100 $finish;
end
endmodule
```

### Output Screenshots:

```
student@pessat196:~/Desktop/PES1UG20CS435/lab3$ vvp dout
VCD info: dumpfile dump1.vcd opened for output.
student@pessat196:~/Desktop/PES1UG20CS435/lab3$ vvp MUX2toiout
VCD info: dumpfile dump2.vcd opened for output.
student@pessat196:~/Desktop/PES1UG20CS435/lab3$ vvp MUX4toiout
VCD info: dumpfile dump3.vcd opened for output.
student@pessat196:~/Desktop/PES1UG20CS435/lab3$ gtkwave dump1.vcd

GTKWave Analyzer v3.3.66 (w)1999-2015 BSI


[0] start time.
[186000] end time.
WM Destroy
student@pessat196:~/Desktop/PES1UG20CS435/lab3$ gtkwave dump2.vcd

GTKWave Analyzer v3.3.66 (w)1999-2015 BSI

[0] start time.
[35] end time.
WM Destroy
student@pessat196:~/Desktop/PES1UG20CS435/lab3$ gtkwave dump3.vcd

GTKWave Analyzer v3.3.66 (w)1999-2015 BSI

 [0] start time.
[15] end time.
WM Destroy
student@pessat196:~/Desktop/PES1UG20CS435/lab3$ █
```



2 Implement a 2:1 MUX.

## Program :

### MUX2to1.v :

```
module mux2 (input wire i0, i1, j, output wire o);
    assign o = (j==0)?i0:i1;
endmodule
```

### testBench2to1.v:

```
module TB;
    reg A,B,S;
    wire X;
    initial
    begin
        $dumpfile("dump2.vcd");
        $dumpvars(0,TB);
    end
    mux2 newMUX(.i0(A), .i1(B), .j(S), .o(X));
    initial
    begin
```

	<pre> S = 1'b0; A = 1'b0; B = 1'b0; #5 A = 1'b0; B = 1'b1; #5 A = 1'b1; B = 1'b0; #5 A = 1'b1; B = 1'b1; #5 S = 1'b0; A = 1'b0; B = 1'b0; #5 A = 1'b0; B = 1'b1; #5 A = 1'b1; B = 1'b0; #5 A = 1'b1; B = 1'b1; end endmodule </pre>
	<b>Output Screenshots:</b>

```
student@pessat196:~/Desktop/PES1UG20CS435/lab3$ vvp dout
VCD info: dumpfile dump1.vcd opened for output.
student@pessat196:~/Desktop/PES1UG20CS435/lab3$ vvp MUX2toiout
VCD info: dumpfile dump2.vcd opened for output.
student@pessat196:~/Desktop/PES1UG20CS435/lab3$ vvp MUX4toiout
VCD info: dumpfile dump3.vcd opened for output.
student@pessat196:~/Desktop/PES1UG20CS435/lab3$ gtkwave dump1.vcd

GTKWave Analyzer v3.3.66 (w)1999-2015 BSI


[0] start time.
[186000] end time.
WM Destroy
student@pessat196:~/Desktop/PES1UG20CS435/lab3$ gtkwave dump2.vcd

GTKWave Analyzer v3.3.66 (w)1999-2015 BSI

[0] start time.
[35] end time.
WM Destroy
student@pessat196:~/Desktop/PES1UG20CS435/lab3$ gtkwave dump3.vcd

GTKWave Analyzer v3.3.66 (w)1999-2015 BSI

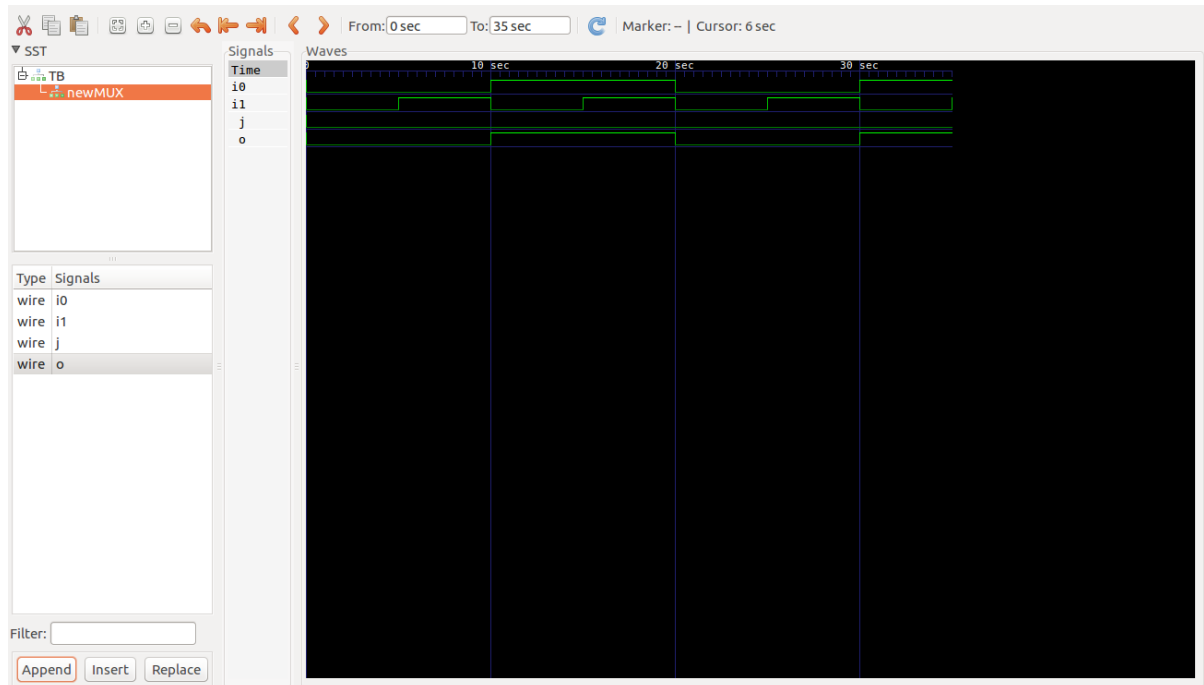[0] start time.
[15] end time.
WM Destroy
student@pessat196:~/Desktop/PES1UG20CS435/lab3$
```



3 Implement a 4:1 MUX using 2:1 MUX modules.

**Program :**

**MUX4to1.v :**

```
module mux2 (input wire i0, i1, j, output wire o);
    assign o = (j==0)?i0:i1;
endmodule

module mux4 (input wire [0:3] i, input wire j1, j0, output wire o);
    wire t0, t1;


    mux2 m1(i[0], i[1], j0, t0);
    mux2 m2(i[2], i[3], j0, t1);

    mux2 m3(t0, t1, j1, o);

endmodule
```

**testBench4to1.v:**

```
module TB;
    reg [0:3]ii;
    reg s0;
    reg s1;
    wire yy;
    initial
    begin
        $dumpfile("dump3.vcd");
        $dumpvars(0, TB);
    end
    mux4 newMUX(.i(ii), .j0(s0), .j1(s1), .o(yy));
    initial
    begin
        ii = 4'b0001;
        s0=1'b0;
        s1=1'b0;
        #5
        ii = 4'b1000;
        #5
        ii = 4'b0001;
        s0=1'b1;
        s1=1'b1;
        #5
    end
endmodule
```

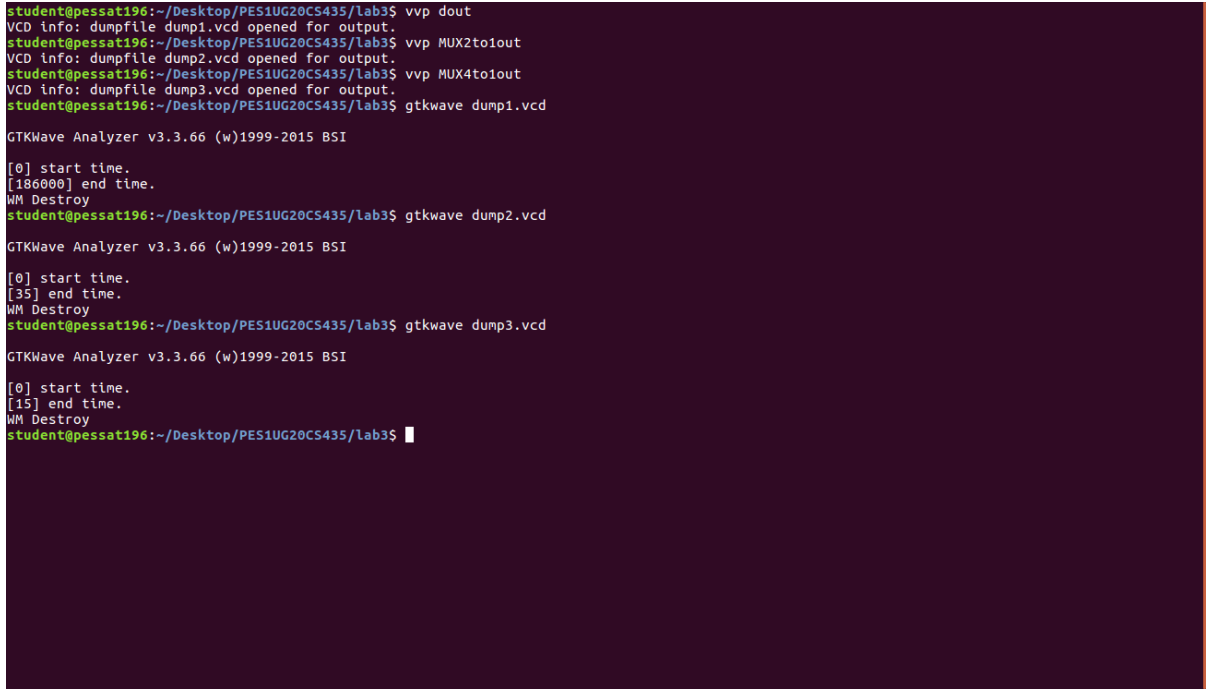	<pre> ii = 4'b0000; s0=1'b1; s1=1'b0; end endmodule </pre>
	<p><b>Output Screenshots:</b></p>  <pre> student@pessat196:~/Desktop/PES1UG20CS435/Lab3\$ vvp dout VCD info: dumpfile dump1.vcd opened for output. student@pessat196:~/Desktop/PES1UG20CS435/Lab3\$ vvp MUX2to1out VCD info: dumpfile dump2.vcd opened for output. student@pessat196:~/Desktop/PES1UG20CS435/Lab3\$ vvp MUX4to1out VCD info: dumpfile dump3.vcd opened for output. student@pessat196:~/Desktop/PES1UG20CS435/Lab3\$ gtkwave dump1.vcd  GTKWave Analyzer v3.3.66 (w)1999-2015 BSI [0] start time. [186000] end time. WM Destroy student@pessat196:~/Desktop/PES1UG20CS435/Lab3\$ gtkwave dump2.vcd  GTKWave Analyzer v3.3.66 (w)1999-2015 BSI [0] start time. [35] end time. WM Destroy student@pessat196:~/Desktop/PES1UG20CS435/Lab3\$ gtkwave dump3.vcd  GTKWave Analyzer v3.3.66 (w)1999-2015 BSI [0] start time. [15] end time. WM Destroy student@pessat196:~/Desktop/PES1UG20CS435/Lab3\$ </pre>



